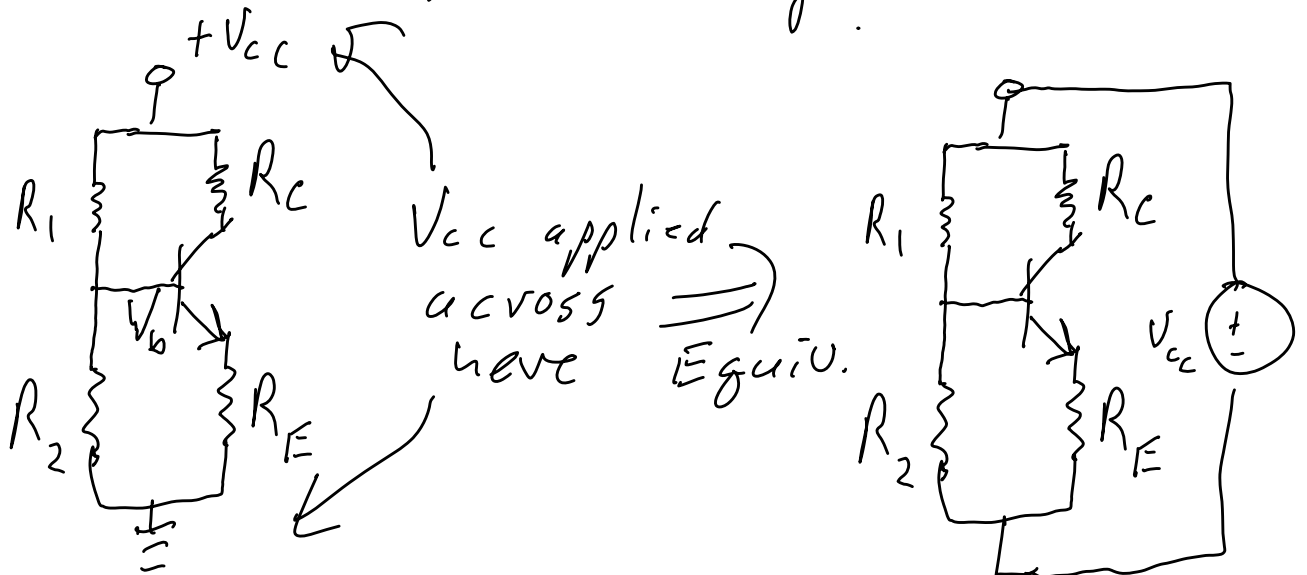


"AC Coupling" (1)

Transistor amplifiers are often "AC coupled" & here I'll explain why. A transistor must be biased before it will work as an amp.

Biasing: Using Resistors & Voltage supplies to establish the needed DC voltages (& currents) to get the transistor "ready" to work as an amp.

Here is a typical biasing circuit:



The goal of this biasing (2) is to ensure that V_b is somewhere around $\frac{V_{cc}}{2}$ so that if we somehow make V_b wiggle up & down... there is room to wiggle:

- if V_b is too close to 0 then can't "wiggle down" very much

- if V_b is too close to V_{cc} then can't "wiggle up" very much


The other goal is to ensure the $V_{be} \approx 0.7V$ & $V_{ce} > 0$

By choosing $R_1, R_2, R_c, \& R_E$ we can do this!

Now we are all set to (3)
inject the signal we want
to amplify...

We must use this signal to
make V_b wiggle up & down.

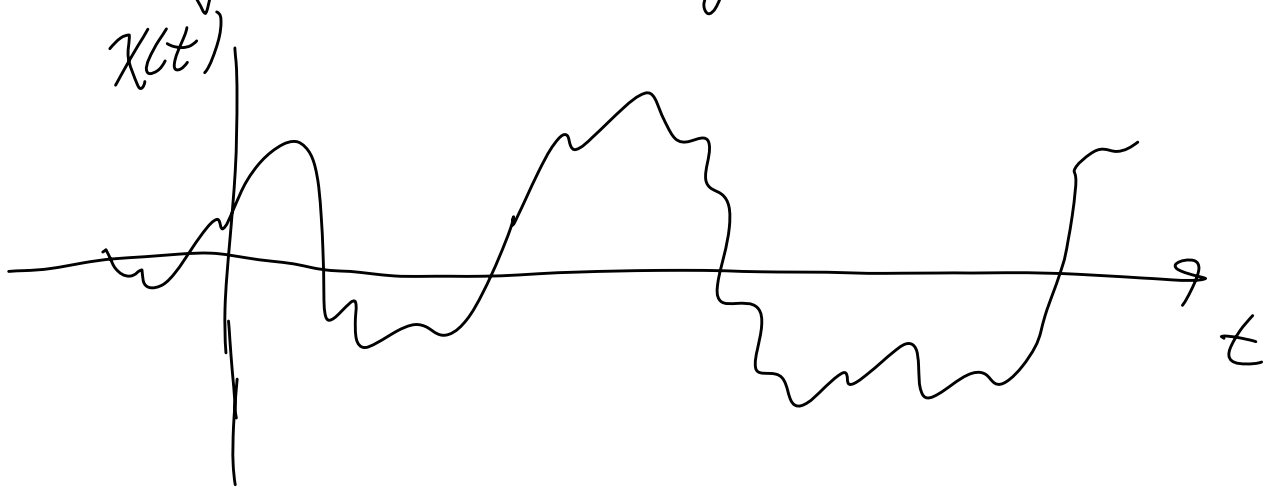Most signals we want to
amplify wiggle around 0V
(e.g. audio signals):




Can we connect this directly
to the V_b point? No!

To see why let's just 4
consider the case of
 $x(t) = \sin(\omega t)$

And... instead of analyzing
the transistor exactly we'll make
some approximations... namely
that the current I_B into the base is
small compared to the current
through R_1 & R_2 .

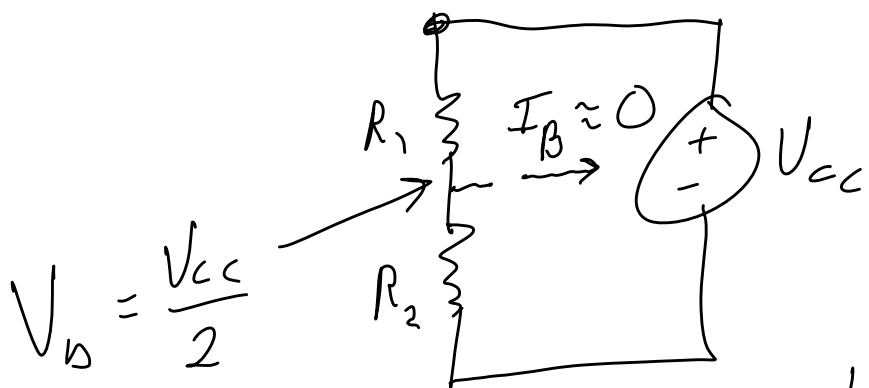Then the "front part" of the biasing
circuit looks like:



We only
need to
analyze this
front part
to see the need
for AC coupling



So... without the sinusoidal (5) signal applied we have $V_B = \frac{V_{CC}}{2}$

When we apply the sinusoid we want

$$V_B(t) = \frac{V_{CC}}{2} + \sin(\omega t)$$

makes V_B wiggle above & below $\frac{V_{CC}}{2}$

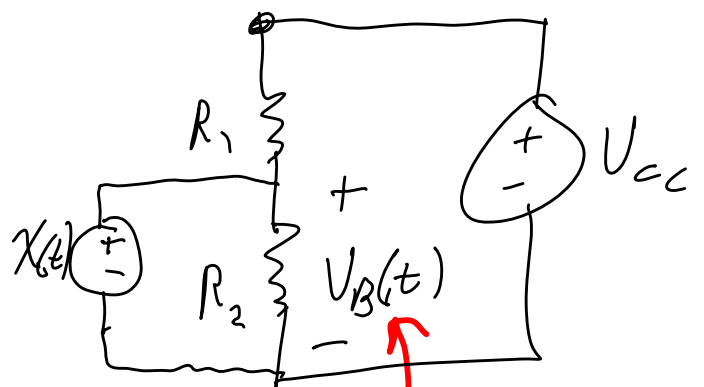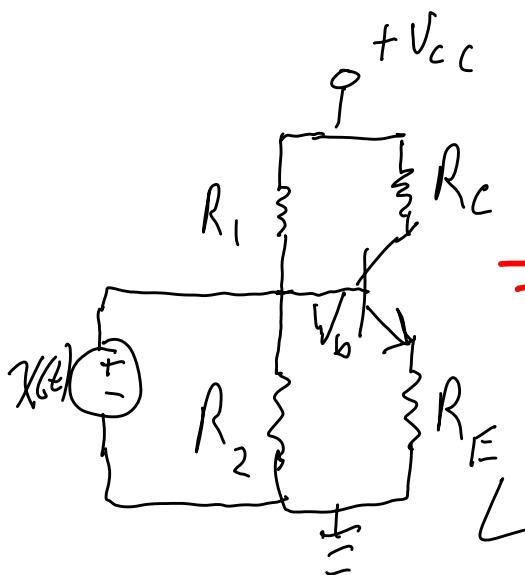Let's see if this works if we directly connect $X(t)$:



Does $V_B(t) = \frac{V_{CC}}{2} + \sin(\omega t)$?


There are many ways to analyze this (Loop, Node, etc.) (6)

We'll use superposition:

- Set the other sources to zero (i.e. short a voltage source, open a current source) and find the response.

- Repeat for each source
- Add all the responses

So...
1. Set $V_{CC} = 0$ (short V_{CC})

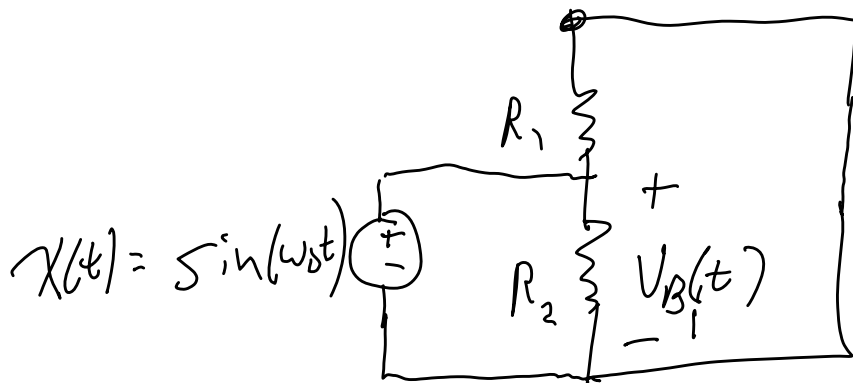


Re-Arranging gives:



$$\Rightarrow V_{B_1}(t) = \sin(\omega t)$$

2. Set $x(t) = 0$ (short it)

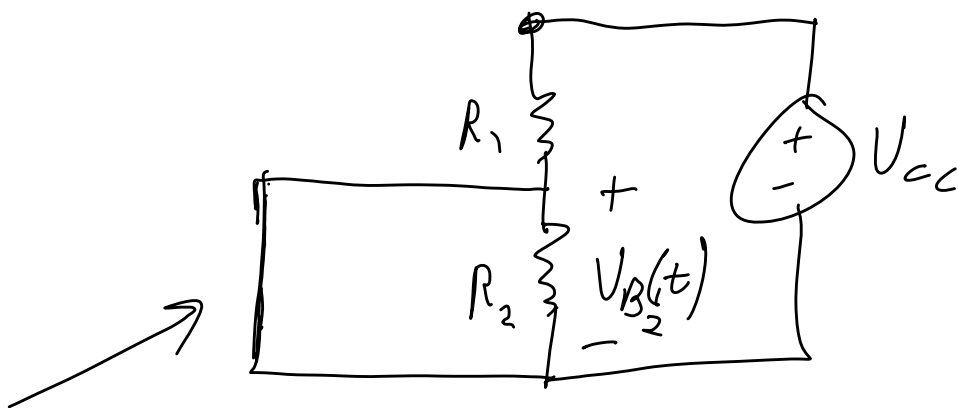

This short across R_2 causes $V_{B_2}(t) = 0$!!

$$\Rightarrow V_B(t) = V_{B_1}(t) + \underbrace{V_{B_2}(t)}_{=0} = \sin(\omega t)$$

Not $\frac{V_{cc}}{2} + \sin(\omega t)$ as desired!



So.... applying $v(t)$ ⑧
directly causes $V_B(t)$ to
go negative which will
reverse bias B-E, which
makes the transistor amp
Not Work!

So how do we Fix This!?

⇒ AC Coupling!!

AC Coupling
used in Actual
Circuit \Rightarrow


Equiv. Ckt.
to analyze
 \downarrow

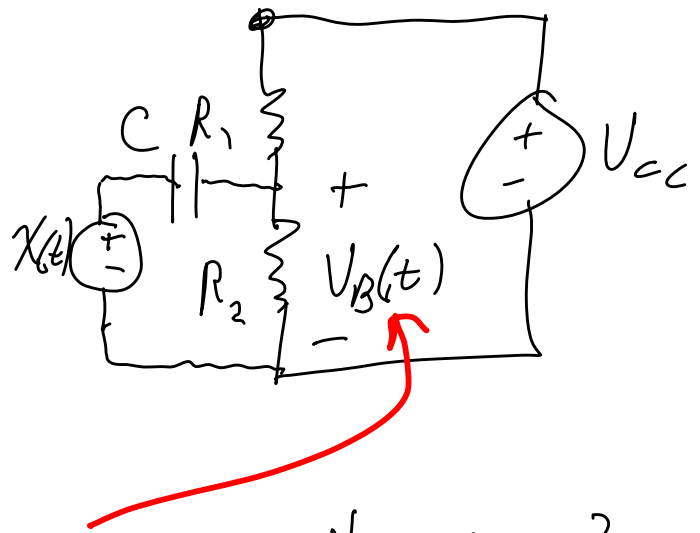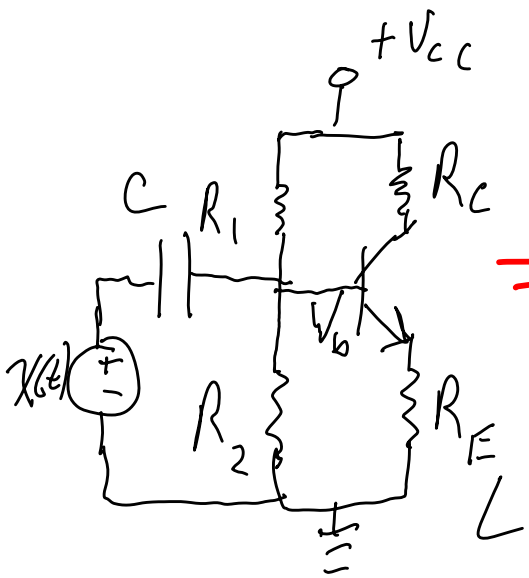


Does $V_B(t) = \frac{V_{CC}}{2} + \sin(\omega t)$?

Now Re-analyze using
superposition:

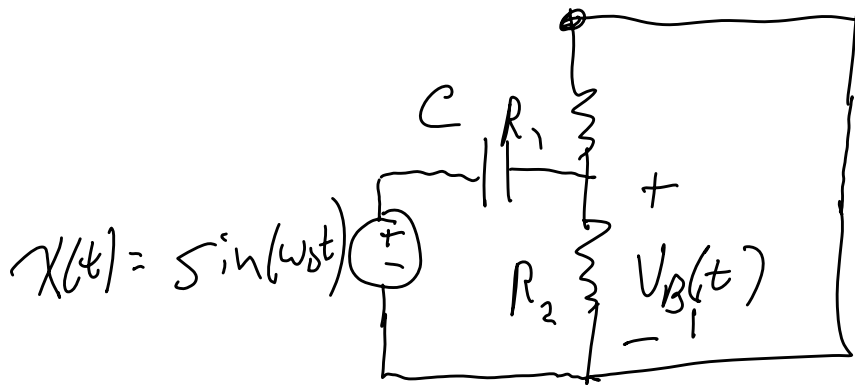
So...
 1. Set $V_{CC} = 0$ (short V_{CC})



Re-arranging gives:

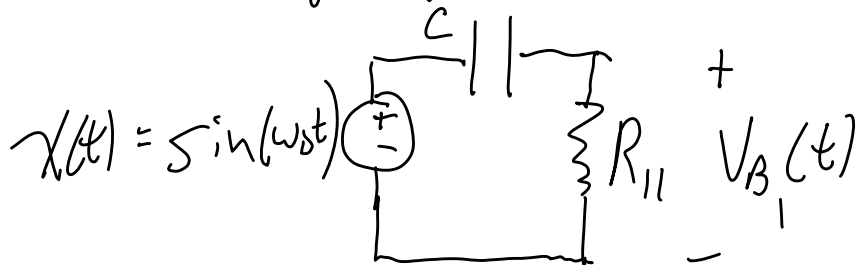


$$R_{11} = R_1 \parallel R_2$$

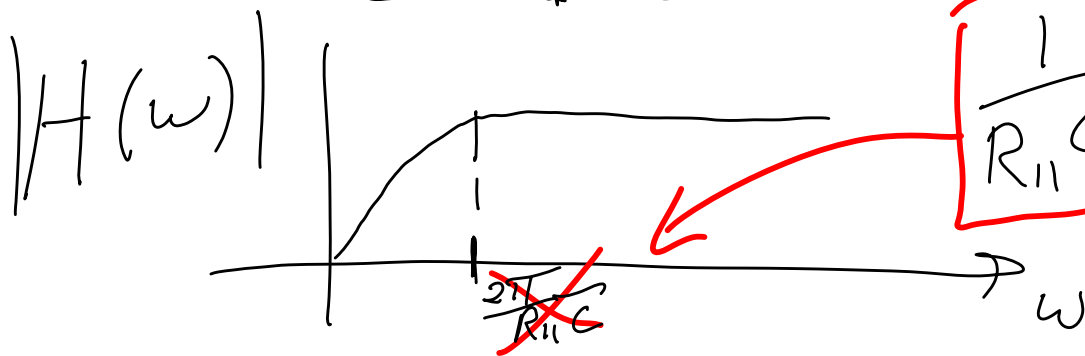


$$\Rightarrow V_{B_1}(t) = \sin(\omega_0 t) \quad \text{if } \frac{1}{R_{11}C} < \omega_0$$

2. Set $X(t) = 0$ (short it)

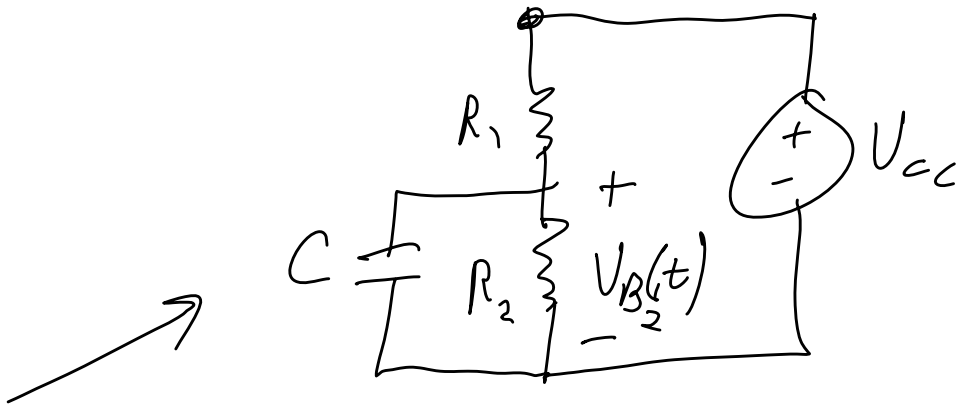

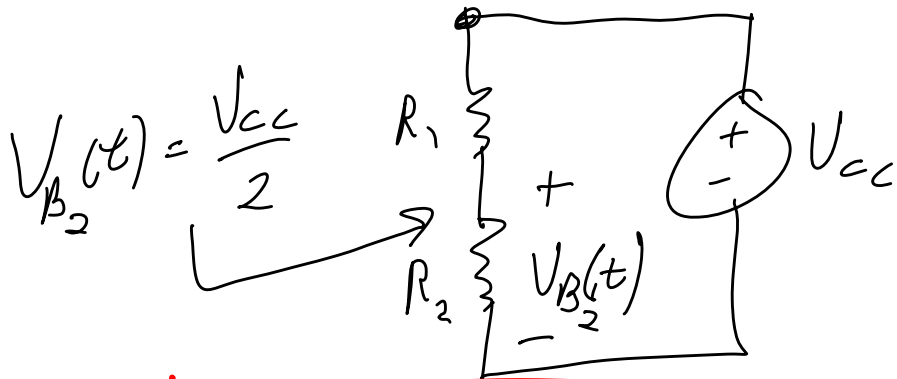This cap. across R_2 causes acts like
open circuit to DC source V_{cc} :



$$\Rightarrow V_B(t) = V_{B_1}(t) + V_{B_2}(t) \\ = \frac{V_{cc}}{2} + \sin(\omega t)$$

AC Coupling Works !!